DOWNLOAD THIS FREE AT

www.vturesource.com

CBCS SCHEME

USN	BESCK104C/ BESCKC10
account of the second of the s	

First Semester B.E./B.Tech. Degree Examination, Jan./Feb. 2023 Introduction to Electronics and Communication

Time: 3 hrs. Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.

2. VTU Formula Hand Book is permitted.

3. M: Marks, L: Bloom's level, C: Course outcomes.

	Module – 1	M	D.	C
Q.1	a. Draw the block diagram of DC power supply and explain the individual blocks.	8	L2	CO1
	b. Draw the circuit diagram of voltage regulation and explain the operation.	6	L2	COI
	c. An amplifier produces an output voltage of 2V for an input of 50mV. If the input and output currents in this condition are 4mA and 200mA respectively. Find: i) The voltage gain ii) The current gain iii) The power gain.	6	L3	COI
	OR A			-
Q.2	a. With a neat circuit diagram and waveform. Explain the working operation of a full wave bridge rectifier.	8	L.2	COI
	b. Draw the circuit diagram of voltage doubler and the working operation.	6	L2	CO1
	c. Discuss briefly a Negative feedback amplifier with block diagram.	6	Li	COI
	Module – 2			
Q.3	a. With circuit diagram, explain the operation of an wien bridge oscillator.	8	1.2	CO2
	b. Define the following operational amplifier parameters value. i) Open loop voltage gain ii) Output Resistance iii) Slew Rate.	6	LI	CO2
	c. Draw the circuit diagram and input and output waveform of the following operational amplifier circuits i) Differentiators ii) Integrator.	6	LI	CO2
	OR		-	
Q.4	a. Explain the single state astable oscillator with circuit diagram.	8	Li	CO2
	b. What is oscillator? And mention condition for oscillations.	6	LI	CO2
	c. Explain the operation of summing amplifier using operational amplifier and write the output equation.	6	L2	CO2
	1.0f2			

DOWNLOAD THIS FREE AT

www.vturesource.com

	Module – 3 BESCK1040	C/ D	ESCI	10104
Q.5	a. Implement full adder using two half adders and one OR gate. Write the equations for Sum and C_{out} .	8	L3	co
	 b. Convert the following numbers to its equivalent numbers and show the steps. i) (10110001101011.1111100000)₂ = (?)₈ ii) (10110001101011.111110010)₂ = (?)₁₆ iii) (1010.011)₂ = (?)₁₀ 	6	1.2	Co.
	c. Using basic Boolean theorems prove i) $(x + y) (x + z) = x + yz$ ii) $xy + xz + y\overline{z} = xz + y\overline{z}$	6	L3	CO:
	OR	_	-	
Q.6	 a. Express the Boolean function i) F = A + BC in a sum of minterms form ii) F = xy + xz in a product of maxterms form. 	8	L2	CO3
	b. Subtract the following using 10's complement i) $(72532 - 3250)_{10}$ ii) $(3250 - 72532)_{10}$	6	L2	CO3
	c. Write the step by step procedure to design a combinational circuit.	6	L1	CO:
Q.7	a. What is an Embedded system? Compare Embedded systems with general computer systems.	8	L2	CO
	b. Mention the classification of Embedded system based on complexity and performance.	6	LI	CO
	c. Write a short note on – 7-segment LED display.	6	L2	CO
	OR			
Q.8	a. Discuss the typical embedded system elements.	8	L2	CO
	b. What is the difference between RISC and CISC processors?	6	L1	CO
	c. Write a short note on : i) Transducers ii) Sensors.	6	L2	CO4
	Module – 5	- Automotive		
Q.9	 a. Draw the block diagram of basic communication system and briefly explain the individual blocks. 	10	L2	COS
	b. Discuss the types of communication systems.	5	L2	COS
	e. List the advantages of digital communication over analog communication.	5	L1	COS
	OR			
Q.10	at Define Amplitude and Frequency modulation. Sketch AM and FM waveform.	10	L1	COS
	b. Write a short note on: Amplitude Shift Keying (ASK) modulator and demodulator.	10	L2	CO5

2 of 2